 





(a) Ideal clock waveform



(b) More realistic clock waveform






(c) Register module and its connections

 

(d) Simulated waveforms


Figure 1.6 Reduced clock slopes can cause a register circuit to fail.

   


(a) Two cascaded registers

(b) Simulated waveforms

Figure 1.7 Impact of clock misalignment.

 

(a) Routing through the block

 

(b) Routing around the block

For a current of 100 A, a wire resistance of $1.25 \text{ m}\Omega$ leads to a 5% drop in supply voltage (2.5 V supply)! On the other hand, current demand can change from zero to this peak value within 1nsec which leads to a current variation of 100 GA/sec !

Fundamental Design Metrics

- ❑ Functionality

- ❑ Scalability

- ❑ Cost

 - λ NRE (fixed) costs - design effort

 - λ RE (variable) costs - cost of parts, assembly, test

- ❑ Reliability, robustness

 - λ Noise margins

 - λ Noise immunity

- ❑ Performance

 - λ Speed (delay)

 - λ Power consumption; energy

- ❑ Time-to-market

Cost of Integrated Circuits

❑ NRE (non-recurring engineering) costs

λ Fixed cost to produce the design

- design effort
- design verification effort
- mask generation

λ Influenced by the design complexity and designer productivity

λ More pronounced for small volume products

❑ Recurring costs – proportional to product volume

λ silicon processing (also proportional to chip area)


λ Parts

λ assembly (packaging)

λ test

$$\text{cost per IC} = \text{variable cost per IC} + \frac{\text{fixed cost}}{\text{volume}}$$

Die Cost

 

Single die


Wafer



Going up to 12" (30cm)

From <http://www.amd.com>

Cost per Transistor

 


Recurring Costs

$$\text{variable cost} = \frac{\text{cost of die} + \text{cost of die test} + \text{cost of packaging}}{\text{final test yield}}$$

$$\text{cost of die} = \frac{\text{cost of wafer}}{\text{dies per wafer} \times \text{die yield}}$$
 
$$\text{dies per wafer} = \frac{\pi \times (\text{wafer diameter}/2)^2}{\text{die area}} - \frac{\pi \times \text{wafer diameter}}{\sqrt{2} \times \text{die area}}$$



$$\text{die yield} = (1 + (\text{defects per unit area} \times \text{die area})/\alpha)^{-\alpha}$$


$$\text{die yield (\%)} = \text{No. of good chips per wafer} \times 100 / \text{Total number of chips per wafer}$$

α is a parameter that depends upon the complexity of the manufacturing process and is roughly proportional to the number of masks.

$\alpha = 3$ (a good estimate for today's complex CMOS processes)

A value between 0.5 - 1 defects per cm^2 is typical these days.

$$\text{die cost} = f(\text{die area})^4$$

- Smaller gate \rightarrow higher integration density \rightarrow smaller die size
- Smaller gate 
 - faster
 - less energy
 - less gate capacitance

Yield Example

□ Example

- λ wafer size of 12 inches, die size of 2.5 cm^2 , 1 defects/ cm^2 , $\alpha = 3$ (measure of manufacturing process complexity)
- λ 252 dies/wafer (remember, wafers round & dies square)
- λ die yield of 16%
- λ $252 \times 16\% = \text{only } 40 \text{ dies/wafer die yield !}$

Examples of Cost Metrics (1994)

Chip	Metal layers	Line width	Wafer cost	Defects /cm ²	Area (mm ²)	Dies/wafer	Yield	Die cost
386DX	2	0.90	\$900	1.0	43	360	71%	\$4
486DX2	3	0.80	\$1200	1.0	81	181	54%	\$12
PowerPC 601	4	0.80	\$1700	1.3	121	115	28%	\$53
HP PA 7100	3	0.80	\$1300	1.0	196	66	27%	\$73
DEC Alpha	3	0.70	\$1500	1.2	234	53	19%	\$149
Super SPARC	3	0.70	\$1700	1.6	256	48	13%	\$272
Pentium	3	0.80	\$1500	1.5	296	40	9%	\$417

Reliability


Noise in Digital Integrated Circuits

❑ **Noise** – unwanted variations of voltages and currents at the logic nodes

❑ from two wires placed side by side


λ **capacitive coupling**

 - voltage change on one wire can influence signal on the neighboring wire
- cross talk




λ **inductive coupling**

 - current change on one wire can influence signal on the neighboring wire



❑ from noise on the power and ground supply rails

 
λ can influence signal levels in the gate



Static Gate Behavior

- ❑ Steady-state parameters of a gate – *static behavior* – tell how robust a circuit is with respect to both variations in the manufacturing process and to noise disturbances.
- ❑ Digital circuits perform operations on Boolean variables
 $x \in \{0,1\}$
- ❑ A logical variable is associated with a *nominal voltage level* for each logic state
 
$$1 \Leftrightarrow V_{OH} \text{ and } 0 \Leftrightarrow V_{OL}$$




$$V_{OH} = \overline{V_{OL}}$$
$$V_{OL} = \overline{V_{OH}}$$

- ❑ Difference between V_{OH} and V_{OL} is the *logic* or *signal swing* V_{sw}



DC Operation

Voltage Transfer Characteristic

 


$$\begin{aligned} V_{OH} &= f(V_{OL}) \\ V_{OL} &= f(V_{OH}) \\ V_M &= f(V_M) \end{aligned}$$

  Mapping between analog and digital signals



Noise Margins

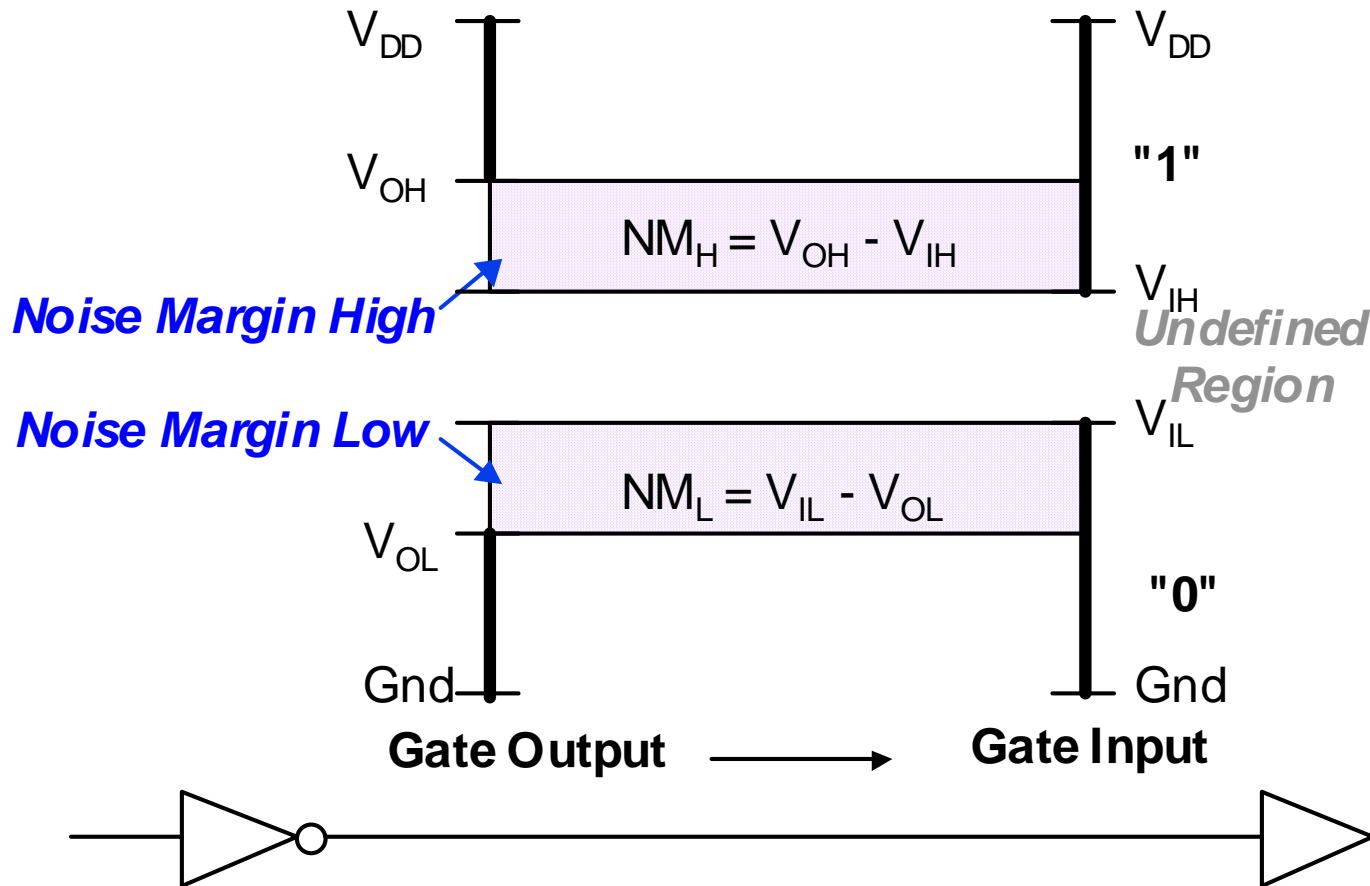- For robust circuits, want the “0” and “1” intervals to be as large as possible



- Large noise margins are desirable, but not sufficient ...

Noise Immunity

- ❑ Noise margin expresses the ability of a circuit to overpower a noise source
 - λ noise sources: supply noise, cross talk, interference, offset
- ❑ Absolute noise margin values are deceptive
 - λ a floating node is more easily disturbed than a node driven by a low impedance (in terms of voltage)
- ❑ *Noise immunity* expresses the ability of the system to process and transmit information correctly in the presence of noise (reject a noise source)
- ❑ For good noise immunity, the signal swing (i.e., the difference between V_{OH} and V_{OL}) and the noise margin have to be large enough to overpower the impact of fixed sources of noise

Assuming $V_{NM} = V_{SW}/2$

$$V_{NM} = \frac{V_{sw}}{2} \geq \sum_i f_i V_{Nfi} + \sum_j g_j V_{sw}$$

Given a set of noise sources, we can derive the minimum signal swing necessary for the system to be operational

$$V_{sw} \geq \frac{2 \sum_i f_i V_{Nfi}}{1 - 2 \sum_j g_j}$$

f = transfer function from noise to signal node

V_{Nf} = amplitude of noise (fixed) source



$g V_{SW}$ = Noise proportional to the signal swing

Key Metrics & Reliability Properties


- ❑ Noise immunity is the more important metric – **the capability to suppress noise sources**
- ❑ A gate must be **undirectional**: changes in an output level should not appear at any unchanging input of the same circuit
 - In real circuits *full* directivity is an illusion (e.g., due to capacitive coupling between inputs and outputs)
- ❑ **output impedance** of the driver and **input impedance** of the receiver
 - ideally, the output impedance of the driver should be zero
 - input impedance of the receiver should be infinity

The Regenerative Property

  
- ❑ A gate with regenerative property ensure that a disturbed signal converges back to a nominal voltage level




Conditions for Regeneration

 
 
$$v_1 = f(v_0) \Rightarrow v_1 = \text{finv}(v_2)$$



Regenerative Gate

 


Nonregenerative Gate

- ❑ To be regenerative, the VTC must have a transient region with a gain **greater** than 1 (in absolute value) bordered by two valid zones where the gain is **smaller** than 1. Such a gate has two stable operating points.

Fan-In and Fan-Out


- ❑ Fan-out – number of load gates connected to the output of the driving gate

λ gates with large fan-out are slower

 


- ❑ Fan-in – the number of inputs to the gate

 λ gates with large fan-in are bigger and slower



The Ideal Inverter

 - ❑ The ideal gate should have
 - λ infinite gain in the transition region
 - λ a gate threshold located in the middle of the logic swing
 - λ high and low noise margins equal to half the swing
 - λ input and output impedances of infinity and zero, resp.




$$R_i = \infty$$

$$R_o = 0$$




$$\text{Fanout} = \infty$$

$$NM_H = NM_L = V_{DD}/2$$



An Old-time Inverter

 



Delay Definitions

   

Delay Definitions

  

Ring Oscillator

  


$$T = 2 \times t_p \times N$$

$$2Nt_p \gg t_f + t_r$$

Modeling Propagation Delay

 - Model circuit as first-order RC network



$$V_{out}(t) = (1 - e^{-t/\tau})V$$

$$\text{where } \tau = RC$$

Time to reach 50% point is

$$t = \ln(2) \tau = 0.69 \tau$$

Time to reach 90% point is

$$t = \ln(9) \tau = 2.2 \tau$$

- Matches the delay of an inverter gate

Power Dissipation

- Instantaneous power:

$$p(t) = v(t)i(t) = V_{supply}i(t)$$

- supply line sizing (determined by **peak power**)

Peak power:

$$P_{peak} = V_{supply}i_{peak}$$

- battery lifetime (determined by **average power dissipation**)

Average power:

$$P_{ave} = \frac{1}{T} \int_t^{t+T} p(t)dt = \frac{V_{supply}}{T} \int_t^{t+T} i_{supply}(t)dt$$

- packaging and cooling requirements

Power and Energy Dissipation

- ❑ Propagation delay and the power consumption of a gate are related
- ❑ Propagation delay is (mostly) determined by the speed at which a given amount of energy can be stored on the gate capacitors
 - λ the faster the energy transfer (higher power dissipation) the faster the gate
- ❑ For a given technology and gate topology, the product of the power consumption and the propagation delay is a constant
 - λ **Power-delay product (PDP)** – energy consumed by the gate per switching event : $P_{av} \times t_p$
- ❑ An ideal gate is one that is fast and consumes little energy, so the ultimate quality metric is
 - λ **Energy-delay product (EDP)** = $PDP \times t_p$

Power and Energy Dissipation

□ Two important components: **static** and **dynamic**

$$E \text{ (joules)} = C_L V_{dd}^2 P_{0 \rightarrow 1} + t_{sc} V_{dd} I_{peak} P_{0 \rightarrow 1} + V_{dd} I_{leakage}$$

$$\downarrow \quad f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock} \quad \downarrow$$

$$P \text{ (watts)} = C_L V_{dd}^2 f_{0 \rightarrow 1} + t_{sc} V_{dd} I_{peak} f_{0 \rightarrow 1} + V_{dd} I_{leakage}$$

$$PDP = C_L V_{dd}^2 f_{0 \rightarrow 1} t_p$$

$$E_{0 \rightarrow 1} = \int_0^T P(t) dt = V_{dd} \int_0^T i_{supply}(t) dt = V_{dd} \int_0^{V_{dd}} C_L dV_{out} = C_L \cdot V_{dd}^2$$

$$E_{cap} = \int_0^T P_{cap}(t) dt = \int_0^T V_{out} i_{cap}(t) dt = \int_0^{V_{dd}} C_L V_{out} dV_{out} = \frac{1}{2} C_L \cdot V_{dd}^2$$