

 


# *The CMOS Inverter: A First Glance*


 


# CMOS Inverter

 


# CMOS Inverter:

## Steady State Response

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

# CMOS Inverter: Transient Response

 

(a) Low-to-high

 

(b) High-to-low


$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$

# CMOS Properties

---

- ❑ Full rail-to-rail swing  $\Rightarrow$  high noise margins
  - Logic levels not dependent upon the relative device sizes  $\Rightarrow$  transistors can be minimum size  $\Rightarrow$  ratioless
- ❑ Always a path to  $V_{dd}$  or GND in steady state  $\Rightarrow$  low output impedance (output resistance in  $k\Omega$  range)  $\Rightarrow$  large fan-out (less sensitive to noise as well)
- ❑ Extremely high input resistance (gate of MOS transistor is near perfect insulator)  $\Rightarrow$  nearly zero steady-state input current
- ❑ No direct path steady-state between power and ground  $\Rightarrow$  no static power dissipation
- ❑ Propagation delay function of load capacitance and resistance of transistors (limits fan-out)


# Review: Short Channel I-V Plot (NMOS)

 

NMOS transistor,  $0.25\mu\text{m}$ ,  $L_d = 0.25\mu\text{m}$ ,  $W/L = 1.5$ ,  $V_{DD} = 2.5\text{V}$ ,  $V_T = 0.4\text{V}$
 
## Review: Short Channel I-V Plot (PMOS)

- All polarities of all voltages and currents are reversed



PMOS transistor,  $0.25\mu\text{m}$ ,  $L_d = 0.25\mu\text{m}$ ,  $W/L = 1.5$ ,  $V_{DD} = 2.5V$ ,  $V_T = -0.4V$



# Transforming PMOS I-V Lines

- Want common coordinate set  $V_{in}$ ,  $V_{out}$ , and  $I_{Dn}$  (load-line plot)

$$I_{DSp} = -I_{DSn}$$


$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$
 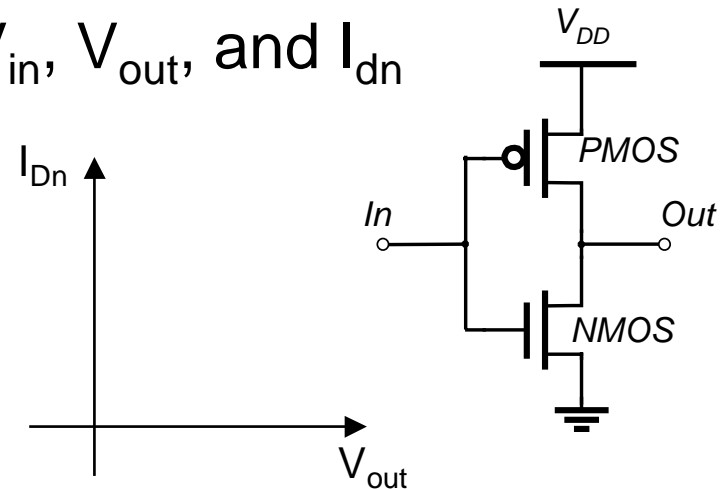
$$V_{DSn} = V_{out} ; V_{DSp} = V_{out} - V_{DD}$$






# CMOS Inverter Load Lines

 

0.25 $\mu$ m,  $W/L_n = 1.5$ ,  $W/L_p = 4.5$ ,  $V_{DD} = 2.5V$ ,  $V_{Tn} = 0.4V$ ,  $V_{Tp} = -0.4V$

# CMOS Inverter VTC

 

The response of the inverter is dominated mainly by the output capacitance of the gate  $C_L$ , which is composed of:

- Drain diffusion capacitance of PMOS & NMOS transistors
- Capacitances of connecting wires
- Input capacitance of the fan-out gates

A fast gate is built either by keeping the output capacitance small or by decreasing the on-resistance of the transistor. The latter is achieved by increasing the  $W/L$  ratio.

# Relative Transistor Sizing

---

- When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
  - maximize the noise margins and
  - obtain symmetrical characteristics

# Switching Threshold as a function of Transistor Ratio

In the transition region both PMOS and NMOS transistors are always saturated, since  $V_{DS} = V_{GS}$ . By equating the currents through the transistors (assuming velocity saturation and ignoring channel length modulation):  $V_{in} = V_{out} = V_M$ ,  $V_{GS} = V_M$  (NMOS),  $V_{GS} = V_M - V_{DD}$  (PMOS)

$$k_n V_{DSATn} \left( V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left( V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) = 0$$

Solving for  $V_M$  yields

$$V_M = \frac{\left( V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left( V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r} \quad \text{with} \quad r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$

# Switching Threshold

□  $V_M$  where  $V_{in} = V_{out}$  (both PMOS and NMOS in saturation since  $V_{DS} = V_{GS}$ ). For large values of  $V_{DD}$  (wrt threshold & saturation voltages):

$$V_M \approx rV_{DD}/(1 + r) \text{ where } r = k_p V_{DSATp}/k_n V_{DSATn}$$

□ Switching threshold set by the ratio  $r$ , which compares the **relative driving strengths** of the PMOS and NMOS transistors

For  $V_M$  to be at  $V_{DD}/2$ ,  $r \approx 1$  which is equivalent to sizing the PMOS device so that:

$$(W/L)_p = (W/L)_n \times (V_{DSATn} k'_n)/(V_{DSATp} k'_p)$$

To move  $V_M$  upwards, a larger value of  $r$  is required, which means making PMOS wider.

The required ratio of PMOS to NMOS transistor sizes such that switching threshold is set to a desired value  $V_M$

$$\frac{(W / L)_p}{(W / L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn} / 2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp} / 2)}$$

For long channel devices or when supply voltage is low (no velocity saturation):

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}, \quad r = \sqrt{\frac{-k_p}{k_n}}$$

# Switching Threshold Example

- ❑ In our generic 0.25 micron CMOS process, using the process parameters  $V_{DD} = 2.5V$ , and a minimum size NMOS device  $((W/L)_n$  of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	$115 \times 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \times 10^{-6}$	-0.1


For  $V_M = 1.25V$  (half of  $V_{DD}$ ):

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$



# Simulated Inverter $V_M$

 





Note: x-axis is semilog

□  $V_M$  is relatively insensitive to variations in device ratio

● setting the ratio to 3, 2.5 and 2 gives  $V_M$ 's of 1.22V, 1.18V, and 1.13V

□ Increasing the width of the PMOS moves  $V_M$  towards  $V_{DD}$

    
□ Increasing the width of the NMOS moves  $V_M$  toward GND



a) Response of standard inverter

b) Response of modified threshold
 
# Noise Margins Determining $V_{IH}$ and $V_{IL}$



A piece-wise linear approximation of VTC

By definition,  $V_{IH}$  and  $V_{IL}$  are where  $dV_{out}/dV_{in} = -1$  (= gain)

$$V_{IH} - V_{IL} = -(V_{OH} - V_{OL})/g = -V_{DD}/g$$

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL} - GND$$


Approximating:

$$V_{IH} = V_M - V_M/g$$

$$V_{IL} = V_M + (V_{DD} - V_M)/g$$

So high gain in the transition region is very desirable

# Gain Determinates

 


Gain is a strong function of the slopes of the currents in the saturation region, for  $V_{in} = V_M$

$$dV_{out}/dV_{in} = g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$

$$\approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$



Determined by technology parameters, especially channel length modulation ( $\lambda$ ). Only designer influence through **supply voltage** and  $V_M$  (**transistor sizing**).
 
# Impact of Process Variation on VTC Curve



rocess variations (mostly) cause a shift in the switching threshold


# *Gain as a function of $V_{DD}$*

  

## Why don't we operate at low supply voltages?


- Reducing the supply voltage improves gain and energy dissipation. But severely degrades the delay of the gate
- The dc characteristic becomes increasingly sensitive to variations in the device parameters
- While it helps to reduce the internal noise (such as crosstalk), it makes the device more sensitive to external noise sources that do not scale.

To achieve sufficient gain for use in a digital circuit, it is necessary that the supply be at least  $4\phi_T$  where  $\phi_T = kT/q$  (the only way to operate CMOS inverters below 100mV is to reduce the ambient temperature, that is to cool the circuit)

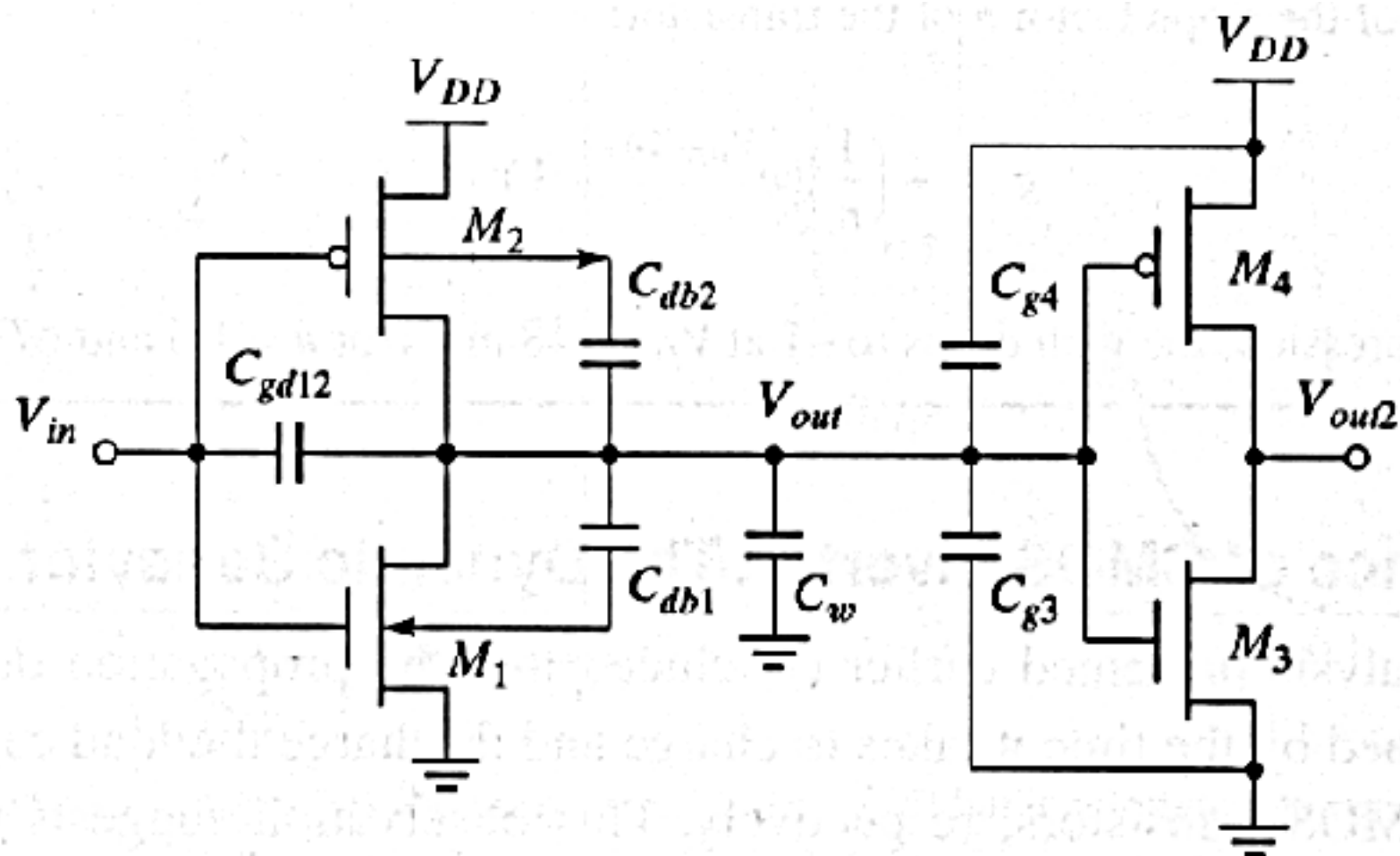

**Figure 5-13** Parasitic capacitances, influencing the transient behavior of the cascaded inverter pair.



 

**Figure 5-14** The Miller effect—A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.

Diffusion capacitances  $C_{db1}$  and  $C_{db2}$

$$C_{eq} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-\Phi_0^m}{(V_{high} - V_{low})(1-m)} \left[ (\Phi_0 - V_{high})^{1-m} - (\Phi_0 - V_{low})^{1-m} \right]$$

voltage swing goes from rail to rail or equals 2.5 V. We therefore linearize the junction capacitance over the interval  $\{2.5 \text{ V}, 1.25 \text{ V}\}$  for the high-to-low transition, and  $\{0, 1.25 \text{ V}\}$  for the low-to-high transition.

During the high-to-low transition at the output,  $V_{out}$  initially equals 2.5 V. Because the bulk of the NMOS device is connected to  $GND$ , this translates into a reverse voltage of 2.5 V over the drain junction or  $V_{high} = -2.5 \text{ V}$ . At the 50% point,  $V_{out} = 1.25 \text{ V}$  or  $V_{low} = -1.25 \text{ V}$ . Evaluating Eq. (5.14) for the bottom plate and sidewall components of the diffusion capacitance yields the following data:

$$\text{Bottom plate: } K_{eq} (m = 0.5, \phi_0 = 0.9) = 0.57$$

$$\text{Sidewall: } K_{eqsw} (m = 0.44, \phi_0 = 0.9) = 0.61$$

During the low-to-high transition,  $V_{low}$  and  $V_{high}$  equal 0 V and  $-1.25 \text{ V}$ , respectively, resulting in higher values for  $K_{eq}$ :

$$\text{Bottom plate: } K_{eq} (m = 0.5, \phi_0 = 0.9) = 0.79$$

$$\text{Sidewall: } K_{eqsw} (m = 0.44, \phi_0 = 0.9) = 0.81$$

The PMOS transistor displays a reverse behavior, as its substrate is connected to 2.5 V. Hence, for the high-to-low transition ( $V_{low} = 0$ ,  $V_{high} = -1.25 \text{ V}$ ), we have

$$\text{Bottom plate: } K_{eq} (m = 0.48, \phi_0 = 0.9) = 0.79$$

$$\text{Sidewall: } K_{eqsw} (m = 0.32, \phi_0 = 0.9) = 0.86$$

Finally, for the low-to-high transition ( $V_{low} = -1.25 \text{ V}$ ,  $V_{high} = -2.5 \text{ V}$ ), we have

$$\text{Bottom plate: } K_{eq} (m = 0.48, \phi_0 = 0.9) = 0.59$$

$$\text{Sidewall: } K_{eqsw} (m = 0.32, \phi_0 = 0.9) = 0.7$$

## Gate Capacitances of Fan-Out $C_{g3}$ and $C_{g4}$

$$C_{\text{fan-out}} = C_{\text{gate}} (\text{NMOS}) + C_{\text{gate}} (\text{PMOS})$$

$$= (C_{\text{GSO}_n} + C_{\text{GDO}_n} + W_n L_n C_{\text{ox}}) + (C_{\text{GSO}_p} + C_{\text{GDO}_p} + W_p L_p C_{\text{ox}})$$

**Table 5-1** Inverter transistor data.

	<b>W/L</b>	<b>AD (<math>\mu\text{m}^2</math>)</b>	<b>PD (<math>\mu\text{m}</math>)</b>	<b>AS (<math>\mu\text{m}^2</math>)</b>	<b>PS (<math>\mu\text{m}</math>)</b>
NMOS	0.375/0.25	0.3 ( $19 \lambda^2$ )	1.875 ( $15\lambda$ )	0.3 ( $19 \lambda^2$ )	1.875 ( $15\lambda$ )
PMOS	1.125/0.25	0.7 ( $45 \lambda^2$ )	2.375 ( $19\lambda$ )	0.7 ( $45 \lambda^2$ )	2.375 ( $19\lambda$ )

From Table 3-5:


Overlap capacitance:  $\text{CGD0}(\text{NMOS}) = 0.31 \text{ fF}/\mu\text{m}$ ;  $\text{CGDO}(\text{PMOS}) = 0.27 \text{ fF}/\mu\text{m}$

Bottom junction capacitance:  $\text{CJ}(\text{NMOS}) = 2 \text{ fF}/\mu\text{m}^2$ ;  $\text{CJ}(\text{PMOS}) = 1.9 \text{ fF}/\mu\text{m}^2$

Sidewall junction capacitance:  $\text{CJSW}(\text{NMOS}) = 0.28 \text{ fF}/\mu\text{m}$ ;  $\text{CJSW}(\text{PMOS}) = 0.22 \text{ fF}/\mu\text{m}$

Gate capacitance:  $C_{\text{ox}}(\text{NMOS}) = C_{\text{ox}}(\text{PMOS}) = 6 \text{ fF}/\mu\text{m}^2$

# CMOS Inverters

 

**Table 5-2** Components of  $C_L$  (for high-to-low and low-to-high transitions).

Capacitor	Expression	Value (fF) (H $\rightarrow$ L)	Value (fF) (L $\rightarrow$ H)
$C_{gd1}$	$2\text{ CGD0}_n W_n$	0.23	0.23
$C_{gd2}$	$2\text{ CGD0}_p W_p$	0.61	0.61
$C_{db1}$	$K_{eqn} AD_n CJ + K_{eqsw_n} PD_n CJSW$	0.66	0.90
$C_{db2}$	$K_{eqp} AD_p CJ + K_{eqsw_p} PD_p CJSW$	1.5	1.15
$C_{g3}$	$(\text{CGD0}_n + \text{CGSO}_n) W_n + C_{ox} W_n L_n$	0.76	0.76
$C_{g4}$	$(\text{CGD0}_p + \text{CGSO}_p) W_p + C_{ox} W_p L_p$	2.28	2.28
$C_w$	From Extraction	0.12	0.12
$C_L$	$\Sigma$	6.1	6.0


# PRORAGATION DELAY

$$I = C \frac{dV}{dt} \quad dt = \frac{C}{I} dV \quad t_p = \int_{V_1}^{V_2} \frac{C_L}{i} dV$$

both  $C_L$  and  $i$  are nonlinear functions of  $V$  an exact computation of this equation is very difficult. Instead, we use the simplified switch model.

$$v_{\text{out}}(t) = (1 - e^{-t/\tau})V$$


$$\text{where } \tau = RC$$

 

Time to reach 50% point is  
 $t = \ln(2) \tau = 0.69 \tau$

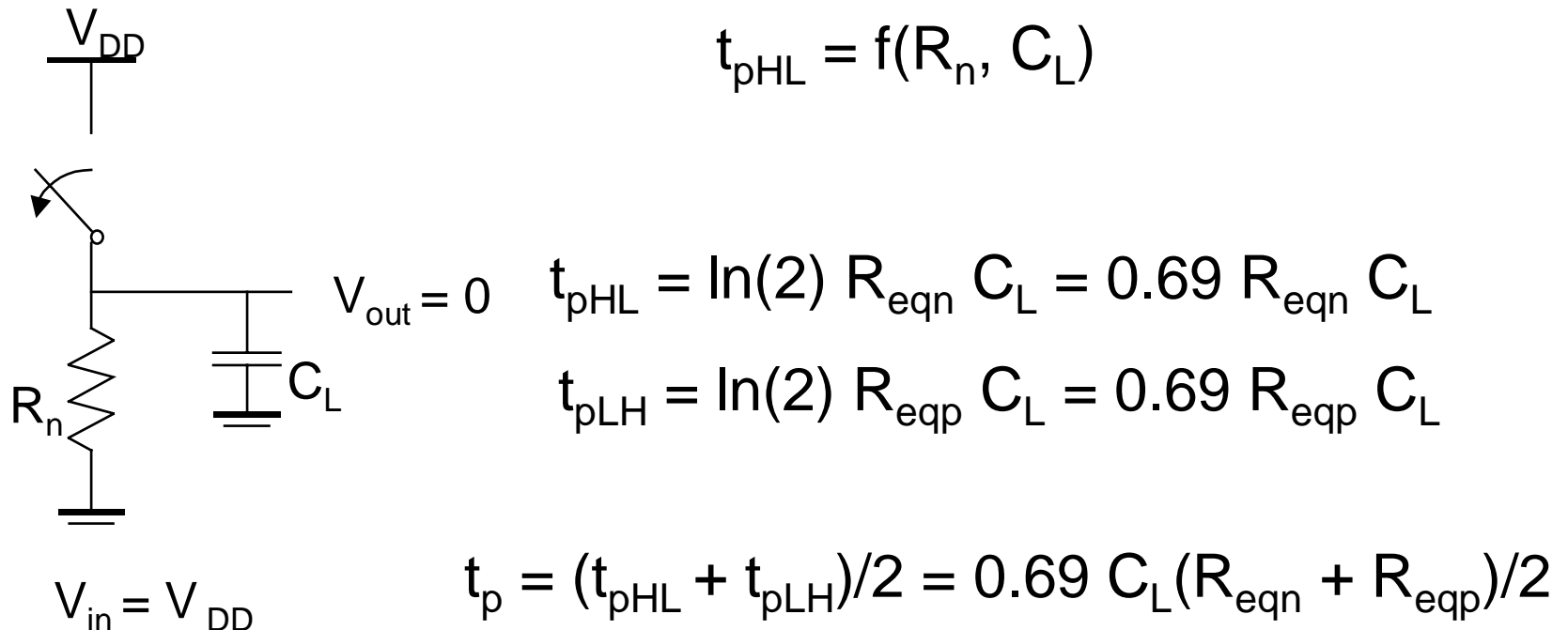
# Inverter Propagation Delay

- Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance




- To equalize rise and fall times make the on-resistance of the NMOS and PMOS approximately equal.

# Transient Response

 



# Inverter Transient Response

 

$$V_{DD} = 2.5V$$

$$0.25\mu m$$

$$W/L_n = 1.5$$

$$W/L_p = 4.5$$

$$R_{eqn} = 13 \text{ k}\Omega (\div 1.5)$$

$$R_{eqp} = 31 \text{ k}\Omega (\div 4.5)$$

$$t_{pHL} = 0.69 \times 13 / 1.5 \times 6.1$$

$$t_{pLH} = 0.69 \times 31 / 4.5 \times 6$$

$$t_{pHL} = 36 \text{ psec}$$


$$t_{pLH} = 29 \text{ psec}$$

so

$$t_p = 32.5 \text{ psec}$$

From simulation:  $t_{pHL} = 39.9 \text{ psec}$  and  $t_{pLH} = 31.7 \text{ psec}$

# Delay as a function of $V_{DD}$

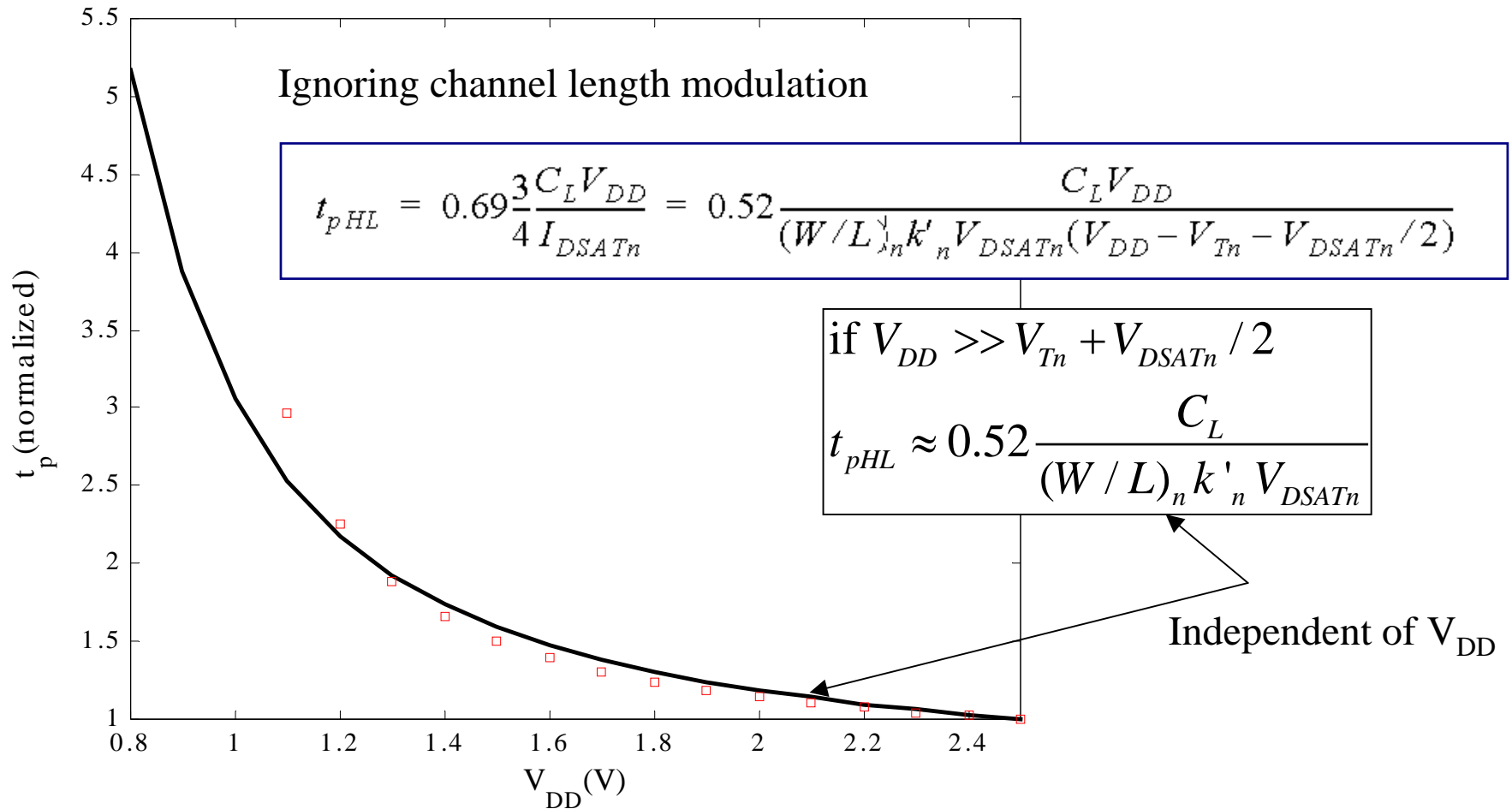

Dots indicate the values calculated. Assumed velocity sat. Deviation at low supply voltages

# Design for Performance

- **Keep capacitances small**  
Good design practice requires keeping the drain diffusion areas as small as possible
- **Increase transistor sizes**  
watch out for self-loading!  
intrinsic capacitance (i.e. diffusion capacitance)  
starts to dominate extrinsic load (wiring & f.out)
- **Increase  $V_{DD}$**   
(????) trade off energy dissipation  
oxide break-down, hot carrier effects  
minimal improvement above a certain level

- So far we have considered widened PMOS so that its resistance matches that of the pull-down NMOS to yield symmetrical VTC.
- However, this does not imply that this ratio also yields the minimum overall propagation delay.
- If symmetry and reduced noise margins are not of prime concern, it is possible to speed up the inverter by reducing the width of the PMOS device.

Consider the 2 identical cascaded CMOS inverters, with approximate load capacitance of the 1. Gate  $C_L$  :

## NMOS to PMOS Ratio

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_w$$

$$\beta = (W/L)_p / (W/L)_n \rightarrow C_{dp1} = \beta C_{dn1}, C_{gp2} = \beta C_{gn2}$$


$$C_L = (1 + \beta)(C_{dn1} + C_{gn2}) + C_w \quad \text{since } t_p = 0.69 C_L \left( \frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$t_p = \frac{0.69}{2} \left[ (1 + \beta)(C_{dn1} + C_{gn2}) + C_w \right] \left( R_{eqn} + \frac{R_{eqp}}{\beta} \right)$$
$$= 0.345 \left[ (1 + \beta)(C_{dn1} + C_{gn2}) + C_w \right] R_{eqn} \left( 1 + \frac{r}{\beta} \right) \quad \text{where, } r = R_{eqp} / R_{eqn}$$

to find the optimal value of  $\beta$ , setting  $\partial t_p / \partial \beta = 0$  we find

$$\beta_{opt} = \sqrt{r \left( 1 + \frac{C_w}{C_{dn1} + C_{gn2}} \right)} \quad \text{or } \beta_{opt} = \sqrt{r} \quad \text{when } C_{dn1} + C_{gn2} \gg C_w$$

# NMOS/PMOS ratio

 

$\beta$  of 2.4 (= 31 k $\Omega$ /13 k $\Omega$ ) gives symmetrical response

$\beta$  of 1.9 gives optimal performance (1.6 calculated)

# NMOS/PMOS Ratio

- ❑ So far have sized the PMOS and NMOS so that the  $R_{eq}$ 's match (ratio of 3 to 3.5)
  - symmetrical VTC
  - equal high-to-low and low-to-high propagation delays
  
- ❑ If speed is the only concern, **reduce** the width of the PMOS device!
  - widening the PMOS degrades the  $t_{pHL}$  due to larger parasitic capacitance

$$\beta = (W/L_p)/(W/L_n)$$

$r = R_{eqp}/R_{eqn}$  (resistance ratio of identically-sized PMOS and NMOS)

$\beta_{opt} = \sqrt{r}$  when wiring capacitance is negligible

**The next question is how transistor sizing (sizing both NMOS and PMOS with the same ratio) impacts the performance of the gate.**

**To answer this question, we must use a sizing factor  $S$ , which relates the transistor sizes of our inverter to a reference gate, typically a minimum sized inverter.**



# Device Sizing for Performance

## □ Divide capacitive load, $C_L$ , into

- $C_{int}$  : intrinsic - diffusion and Miller effect

- $C_{ext}$  : extrinsic - wiring and fanout  $t_p = 0.69 R_{eq} (C_{int} + C_{ext})$

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$


- where  $t_{p0} = 0.69 R_{eq} C_{int}$  is the intrinsic (**unloaded**) delay of the gate ( $C_{ext} = 0$ )

## □ Widening both PMOS and NMOS by a factor **S** reduces $R_{eq}$ by an identical factor ( $R_{eq} = R_{ref}/S$ ), but raises the **intrinsic** capacitance by the same factor ( $C_{int} = SC_{iref}$ )

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0} (1 + C_{ext}/(SC_{iref}))$$

- $t_{p0}$  is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- any  $S$  sufficiently larger than  $(C_{ext}/C_{int})$  yields the best performance gains with least silicon area impact

# Sizing Impacts on Delay

 

The majority of the improvement is already obtained for  $S = 5$ . Sizing factors larger than 10 barely yield any extra gain (and cost significantly more area).

self-loading effect  
(intrinsic capacitance  
dominates)

## Sizing a Chain of Inverters

While sizing up an inverter reduces its delay, it also increases its input capacitance. Gate sizing without taking into account its impact on the delay of the preceding gates is a purely academic enterprise.

Therefore, a more relevant problem is determining the optimum sizing of a gate when **embedded in a real environment**.

# Impact of Fanout on Delay

- ❑ Extrinsic capacitance,  $C_{\text{ext}}$ , is a function of the fanout of the gate - the larger the fanout, the larger the external load.
- ❑ First determine the **input loading** effect of the inverter. Both input gate capacitance  $C_g$  and intrinsic output capacitance  $C_{\text{int}}$  are proportional to the gate sizing, so  $C_{\text{int}} = \gamma C_g$  is independent of gate sizing and


$$t_p = t_{p0} (1 + C_{\text{ext}} / \gamma C_g) = t_{p0} (1 + f / \gamma)$$

i.e., the delay of an inverter is a function of the ratio between its external load capacitance and its input gate capacitance: the **effective fan-out**  $f$

$$f = C_{\text{ext}} / C_g$$
 
# Inverter Chain

- Real goal is to minimize the delay through an inverter chain



the delay of the  $j$ -th inverter stage is ( $C_W$  ignored):

$$t_{p,j} = t_{p0} (1 + C_{g,j+1}/(\gamma C_{g,j})) = t_{p0}(1 + f_j/\gamma)$$

and 
$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

so 
$$t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1}/(\gamma C_{g,j})) , \text{ with } C_{g,N+1}=C_L$$

- If  $C_L$  is given

- How should the inverters be sized?
- How many stages are needed to minimize the delay?

This equation has N-1 unknowns, being  $C_{g,2}$ ,  $C_{g,3}$ , ...  $C_{g,N}$ . The minimum delay can be found by taking N-1 partial derivatives and equating them to zero:

$$\frac{\partial t_p}{\partial C_{g,j}} = 0$$

The result is a set of constraints:

$$\frac{C_{g,j+1}}{C_{g,j}} = \frac{C_{g,j}}{C_{g,j-1}} \quad \text{with } (j=2, \dots, N)$$

In other words, the optimum size of each inverter is the geometric mean of its neighbors sizes:

$$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$$

## Sizing the Inverters in the Chain

- ❑ The optimum size of each inverter is the geometric mean of its neighbors – meaning that if each inverter is sized up by the same factor  $f$  wrt the preceding gate, it will have the same effective fan-out and the same delay

$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$


where  $F$  represents the overall effective fan-out of the circuit ( $F = C_L/C_{g,1} = f^N$ )

and the minimum delay through the inverter chain is

$$t_p = N t_{p0} (1 + (\sqrt[N]{F}) / \gamma)$$

- ❑ The relationship between  $t_p$  and  $F$  is linear for one inverter, square root for two, etc.

## Example of Inverter Chain Sizing

 

- $C_L/C_{g,1}$  has to be evenly distributed over  $N = 3$  inverters

$$C_L/C_{g,1} = 8/1$$

$$f = \sqrt[3]{8} = 2$$



# Determining N: Optimal Number of Inverters

- ❑ What is the optimal value for N given F ( $=f^N$ ) ?
  - if the number of stages is too large, the intrinsic delay of the stages becomes dominant
  - if the number of stages is too small, the effective fan-out of each stage becomes dominant



$$t_p = Nt_{p0} (1 + \sqrt[N]{F} / \gamma)$$

- ❑ The optimum N is found by differentiating the minimum delay expression and setting the result to 0, giving

$$\gamma + \sqrt[N]{F} - \frac{\sqrt[N]{F} \ln F}{N} = 0 \quad \text{or equivalently: } f = e^{(1+\gamma/f)}$$

  
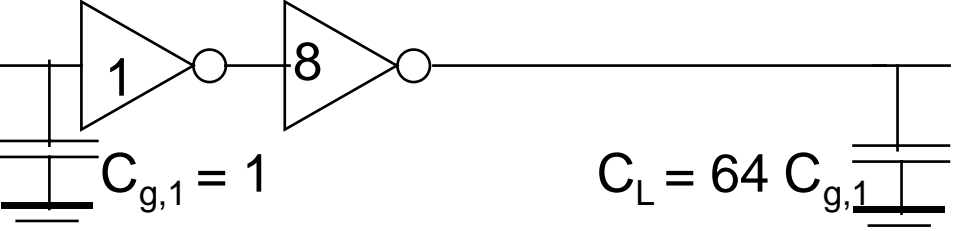
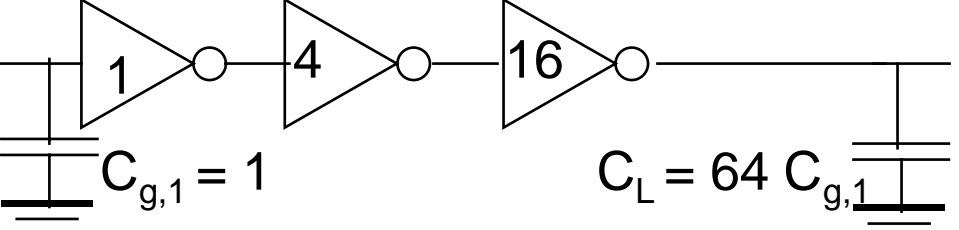
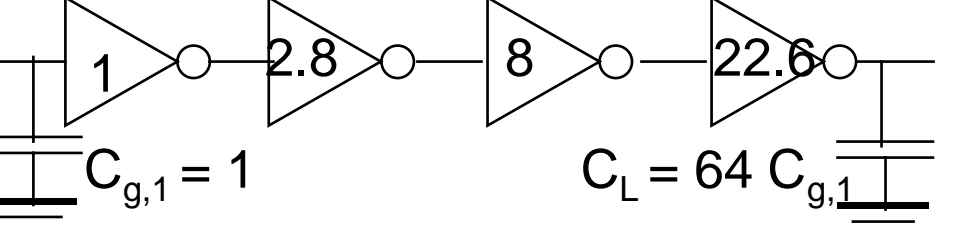
- ❑ For  $\gamma = 0$  (self-loading is ignored)  $N = \ln(F)$  and the effective-fan out becomes  $f = e = 2.71828$
- ❑ For  $\gamma = 1$  (the typical case) the optimum effective fan-out (tapering factor) turns out to be close to 3.6

# Optimum Effective Fan-Out



- ❑ Choosing  $f$  larger than optimum has little effect on delay and reduces the number of stages (and area).
  - Common practice to use  $f = 4$  (for  $\gamma = 1$ )
  - But **too many** stages has a substantial negative impact on delay

# Example of Inverter (Buffer) Staging

	N	f	$t_p$
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>	1	64	65
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>	2	8	18
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>	3	4	15
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>	4	2.8	15.3


## Impact of Buffer Staging for Large $C_L$

<b>F (<math>\gamma = 1</math>)</b>	<b>Unbuffered</b>	<b>Two Stage Chain</b>	<b>Opt. Inverter Chain</b>	<b>N</b>
10	11	8.3	8.3	2
100	101	22	16.5	4
1,000	1001	65	24.8	5
10,000	10,001	202	33.1	7

- ❑ Impressive speed-ups with optimized cascaded inverter chain for very large capacitive loads.
 
# Input Signal Rise/Fall Time

- ❑ In reality, the **input** signal changes gradually (and both PMOS and NMOS conduct for a brief time). This affects the current available for charging/discharging  $C_L$  and impacts propagation delay.
- ❑  $t_p$  increases **linearly** with increasing input slope,  $t_s$ , once  $t_s > t_p$
- ❑  $t_s$  is due to the limited driving capability of the preceding gate



for a minimum-size inverter  
with a fan-out of a single gate

## Design Challenge


- ❑ A gate is never designed in isolation: its performance is affected by both the fan-out and the driving strength of the gate(s) feeding its inputs.

$$t_p^i = t_{\text{step}}^i + \eta t_{\text{step}}^{i-1} \quad (\eta \approx 0.25)$$

- ❑ Keep signal rise times smaller than or equal to the gate propagation delays.
  - good for performance
  - good for power consumption
- ❑ Keeping rise and fall times of the signals small and of approximately equal values is one of the major challenges in high-performance designs - **slope engineering**.
 
# Delay with Long Interconnects

- When gates are farther apart, wire capacitance and resistance can no longer be ignored.



$$t_p = 0.69R_{dr}C_{int} + (0.69R_{dr} + 0.38R_w)C_w + 0.69(R_{dr} + R_w)C_{fan}$$

$$\text{where } R_{dr} = (R_{eqn} + R_{eqp})/2$$

$$= 0.69R_{dr}(C_{int} + C_{fan}) + 0.69(R_{dr}c_w + r_wC_{fan})L + 0.38r_wc_wL^2$$

- Wire delay rapidly becomes the dominate factor (due to the **quadratic term**) in the delay budget for longer wires.